

# CprE 381: Computer Organization and Assembly-Level Programming

## Project Part 2 Report

Team Members:      Conner Ohnesorge  
                             Aidan Foss  
                             Daniel Vergara  
                             Karina Hernandez-Balboa

---


Project Teams Group #: \_\_\_\_\_

*Refer to the highlighted language in the project 1 instruction for the context of the following questions.*


[1.a] Come up with a global list of the datapath values and control signals that are required during each pipeline stage.

IF/ID STAGE		ID/EX STAGE		EX/MEM STAGE		MEM/WB STAGE	
Inputted Signal	New Signals	Inputted Signal	New Signals	Inputted Signal	New Signals	Inputted Signal	New Signals
MemToReg	ReadData1	MemToReg	ALUZero	MemToReg	BranchToMux	MemToReg	MemToRegMux
Branch	ReadData2	Branch	ALUResult	Branch	DataOut	RegWrite	MEMWBRegRD
AluSrc	immExt	AluSrc	AddressToMux	MemWrite	EXMEMRegRD	DataOut	
AluOp		AluOp	FwdBOut	MemRead		ALUResult	
MemWrite		MemWrite	RegisterRD	RegWrite		RegisterRD	
RegWrite		RegWrite		PCSrc			
PCSrc		PCSrc		ALUZero			
RegDst		RegDst		ALUResult			
PC+4		ReadData1		ReadData2			
Imm		ReadData2		FwdBOut			
Address		PC+4		PC+4			
Opcode		immExt		RegisterRD			
rs		rs					
rt		rt					
rd		rd					
shamt		shamt					
funct		funct					

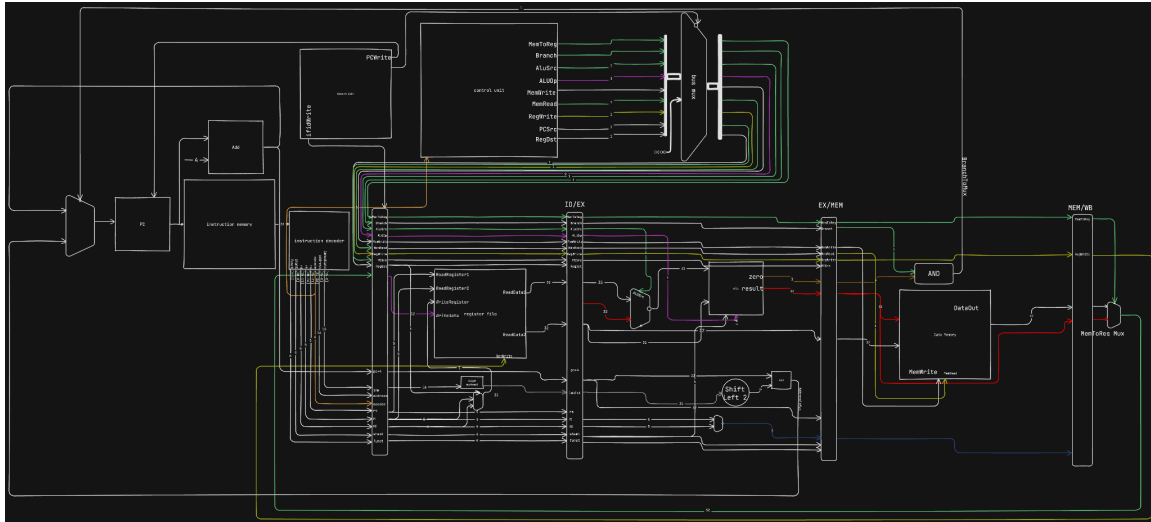[1.b.ii] high-level schematic drawing of the interconnection between components.  
Software Diagram



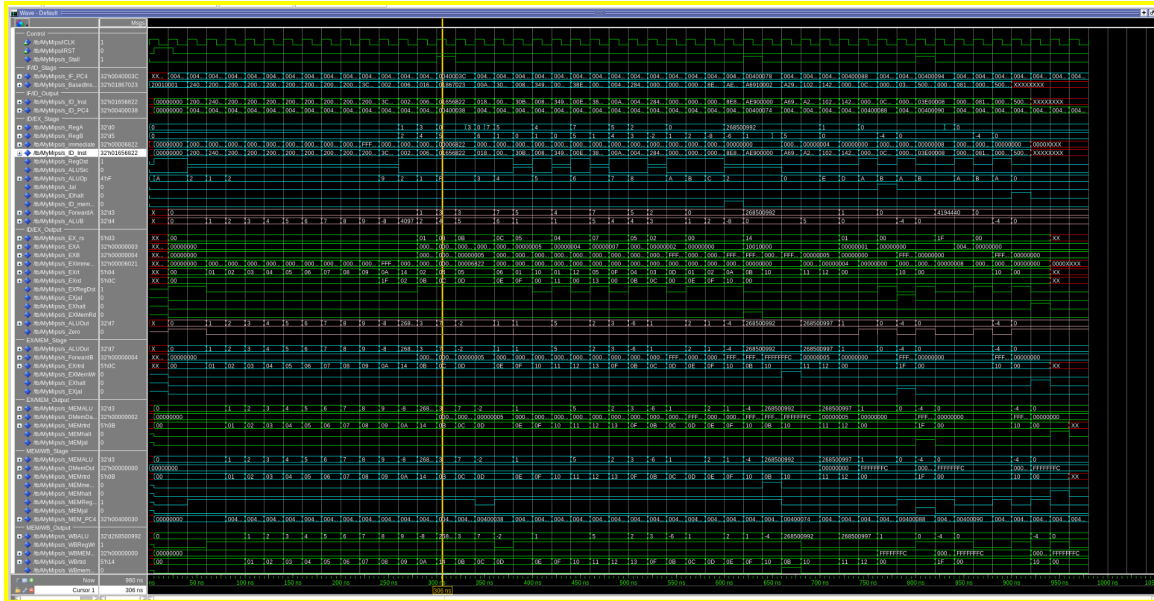[1.c.i] include an annotated waveform in your writeup and provide a short discussion of result correctness.




At the cursor, the fifth instruction listed below is started:

```
add  $11, $1, $2    # $11 = $1 + $2    (1+2 = 3)
addu $12, $3, $4    # $12 = $3 + $4    (3+4 = 7)
nop
nop
sub  $13, $11, $5    # $12 = $11 - $5  (3-5 = -2)
```


The processor correctly ends up with the value -2, shown in pink to the right of the cursor. Using ALUOp 4'hF, or 1111, it subtracts the values and sends them to ALUOut, which is then passed into the input of the next stage in the pipeline. This is used in the stage on the next rising edge, and gets passed down to Mem/Wb, where it gets applied

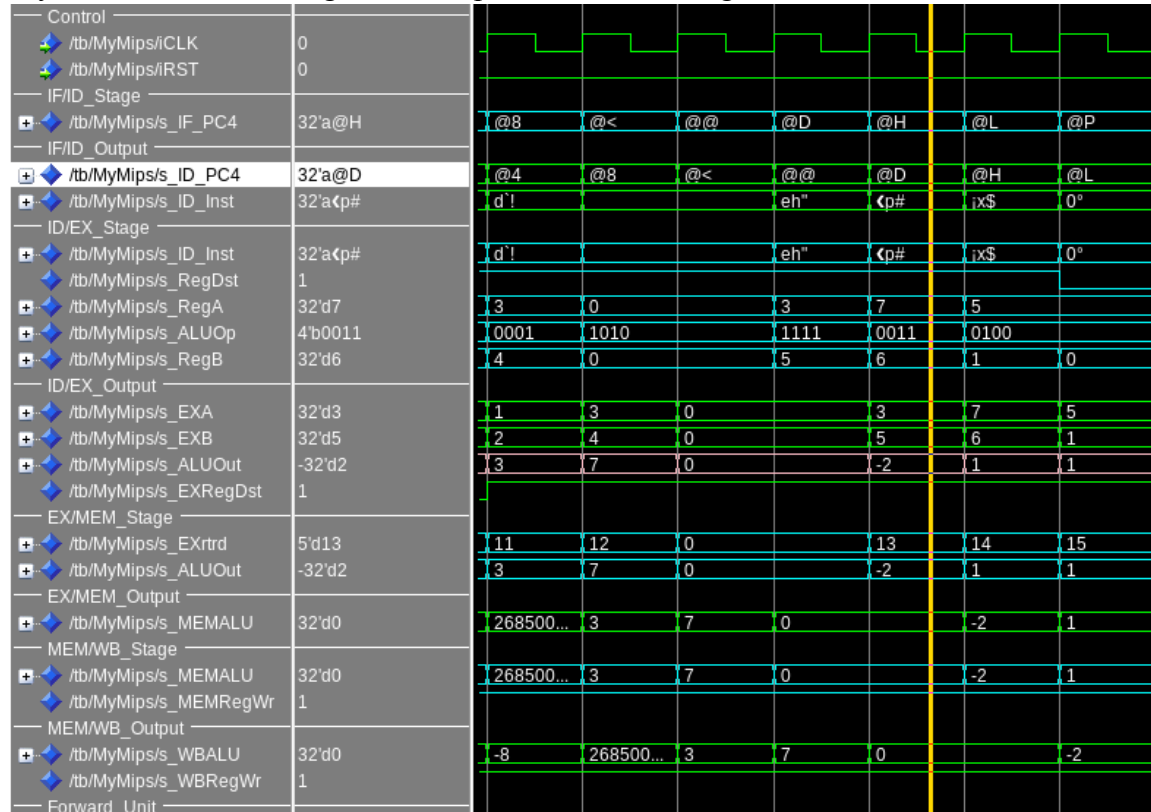Below is a closer look at these instructions. I have some values Radixed to ASCII to show the pipeline properly cycling through each stage. The cursor is hovering over the -2 output of the ALU, and it shows it passing that value down along with RegWrite all the way to the MEM/WB stage as an output at the bottom right.




I named this Proj2\_1ci\_sw.s, and it is implemented for both software and hardware (Proj2\_1ci\_hw.s). The hardware implementation intentionally has 3 instructions that need to be stalled for, which I have nopped in the software implementation.

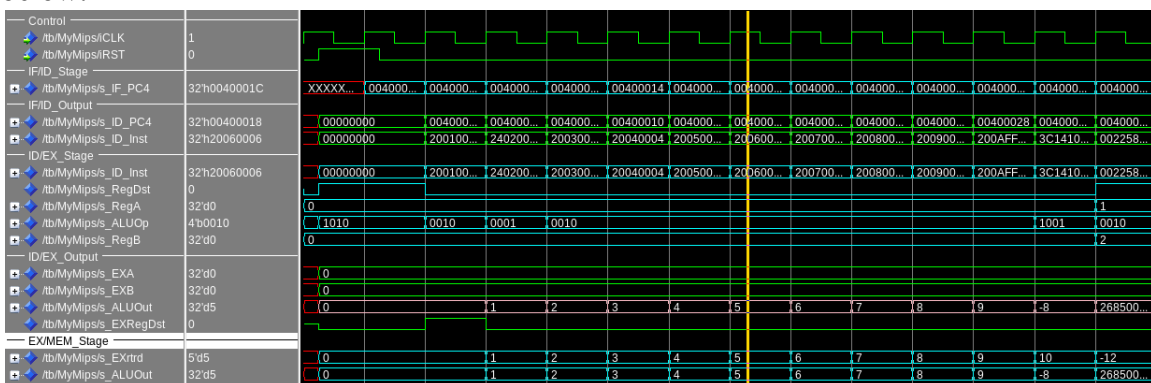The program runs one or more copies of every instruction our processor can currently handle. At the beginning, `addi` is called 10 times, followed immediately by a `lui`, shown below:



 [1.c.ii] Include an annotated waveform in your writeup of two iterations or recursions of these programs (bubblesort) executing correctly and provide a short discussion of result correctness. In your waveform and annotation, provide 3 different examples (at least one data-flow and one control-flow) of where you did not have to use the maximum number of NOPs.



The cursor is hovering over a jump instruction. If you follow the pipeline stages down, separated with dividers, you can see where the jump executes. The following are excerpts from our bubble sort assembly program.

```

.data
.align 2
vals: .word 17 38 20 8008 69 420 100 60 0 12 # address: 0x10010000
vals_length: .word 10 # address: 0x10010028
.text
.globl main

main:
    lui $s1, 0x1001
    lui $s0, 0x1001
    addi $s2, $zero, 0
    nop
    ori $s1, $s1, 0x0028
    nop
    nop
    nop
    lw $s1, 0($s1)
outer_loop_cond:
    nop
    nop
    nop
    addi $t0, $s1, -1
    nop
    nop
    nop
    slt $t1, $s2, $t0
    nop
    nop
    nop
    bne $t1, $zero, outer_loop_body
    nop
    j exit_outer_loop
outer_loop_body:
    add $s4, $zero, $zero
    add $s3, $zero, $zero
inner_loop_cond:
    sub $t0, $s1, $s2
    nop
    nop
    nop
    addi $t0, $t0, -1
    nop
    nop
    nop
    slt $t0, $s3, $t0
    nop
    nop
    nop
    bne $t0, $zero, inner_loop_body
    nop
    nop
    nop
    j exit_inner_loop
    nop
    nop
    nop
inner_loop_body:
    sll $t0, $s3, 2
    nop
    nop
    nop
    add $s5, $s0, $t0
    nop
    nop
    nop
    addi $s6, $s5, 4
    lw $t0, 0($s5)
    nop
    nop
    lw $t1, 0($s6)
    nop
    nop
    nop
    slt $t2, $t1, $t0
    nop
    nop
    nop
    beq $t2, $zero, inner_loop_footer
    nop
    sw $t0, 0($s6)
    sw $t1, 0($s5)
    addi $s4, $zero, 1
inner_loop_footer:
    addi $s3, $s3, 1
    nop
    nop
    nop
    j inner_loop_cond
exit_inner_loop:
    nop
    beq $s4, $zero, exit_outer_loop
outer_loop_footer:
    nop
    addi $s2, $s2, 1
    nop
    nop
    nop
    j outer_loop_cond
    nop
exit_outer_loop:
    j exit
exit:
    halt

```

### 1. Data-Flow Example:

```
```\mips
lw $t0, 0($s5)
nop
nop      # Only 2 NOPs used
lw $t1, 0($s6)
```\
```

Here only 2 NOPs are needed after the load instruction because the value from the first load (\$t0) isn't used immediately by the second load instruction. The second load is independent of the first load's result.

### 2. Control-Flow Example:

```
```\mips
beq $s4, $zero, exit_outer_loop
outer_loop_footer:
nop      # Only 1 NOP used
addi $s2, $s2, 1
```\
```

Only 1 NOP is used here because the branch instruction and increment are independent - the increment operation doesn't affect or depend on the branch condition (\$s4).

### 3. Another Data-Flow Example:

```
```\mips
nop      # Only 2 NOPs used
nop
beq $t2, $zero, inner_loop_footer
```\
```

Before the branch instruction, only 2 NOPs are used because the comparison value in \$t2 was already stable and the branch doesn't require the full 3-NOP delay in this case.

### [For teams with >4]


[1.c.iii] Include an annotated waveform in your writeup of two iterations or recursions of these programs (mergesort) executing correctly and provide a short discussion of result correctness. In your waveform and annotation, provide 3 different examples (at least one data-flow and one control-flow) of where you did not have to use the maximum number of NOPs.

[1.d] report the maximum frequency your software-scheduled pipelined processor can run at and determine what your critical path is (specify each module/entity/component that this path goes through).

```
FMax: 52.86mhz  
From Node      :  
mem:IMem|altsyncram:ram_rtl_0|altsyncram_eg81:auto_generated|ra  
m_block1a0~porta_we_reg  
To Node        : dffg_n:instPC|dffg:\G1:13:flipflop|s_Q
```

Thus, we infer that our critical path is from the PC through the registerfile as we spend over 7ns in that region during instruction fetch. More specifically, our branch/jump detection unit (zero detector) is the slowest part of the instruction fetch process.

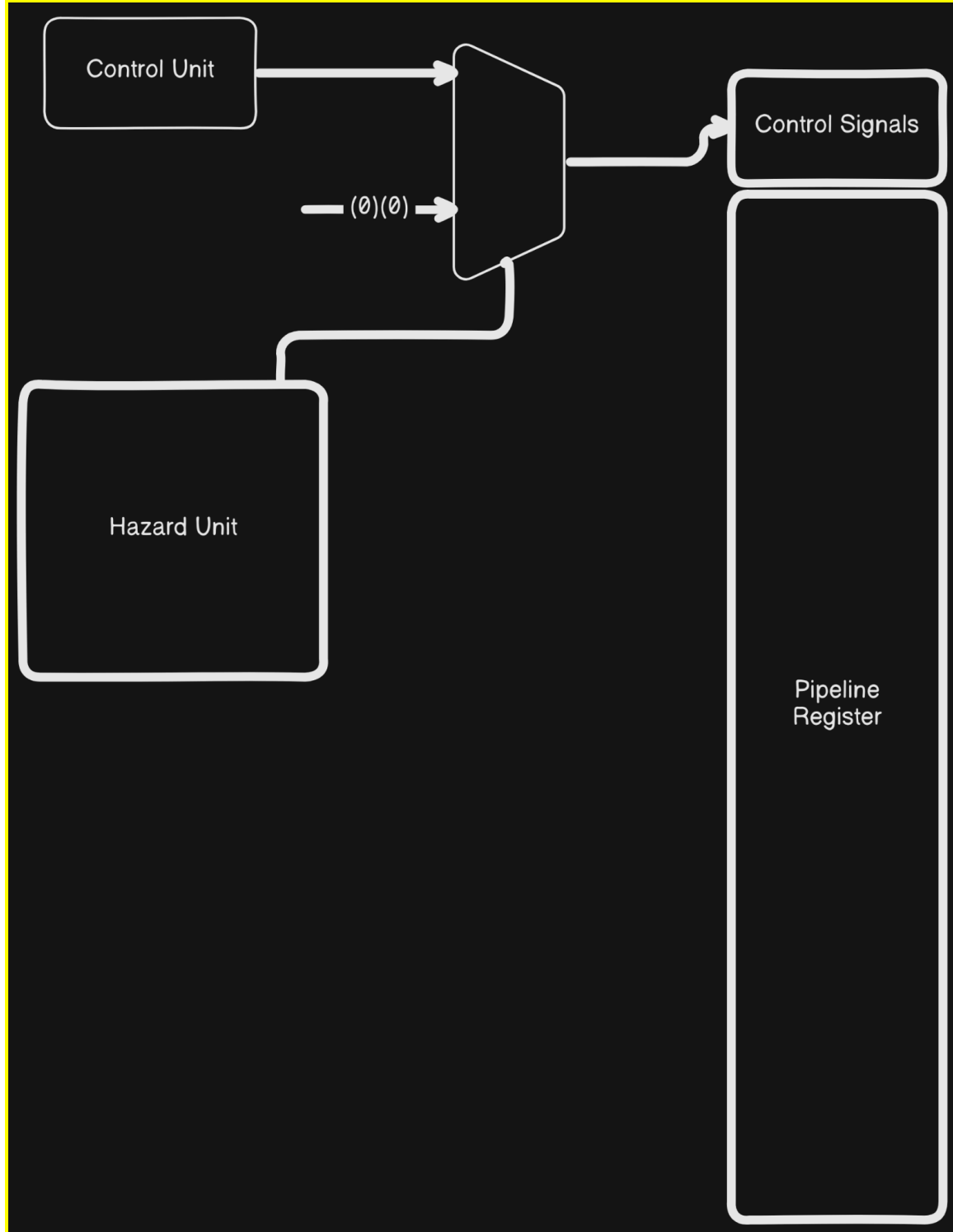
[2.a.ii] Draw a simple schematic showing how you could implement stalling and flushing operations given an ideal N-bit register.



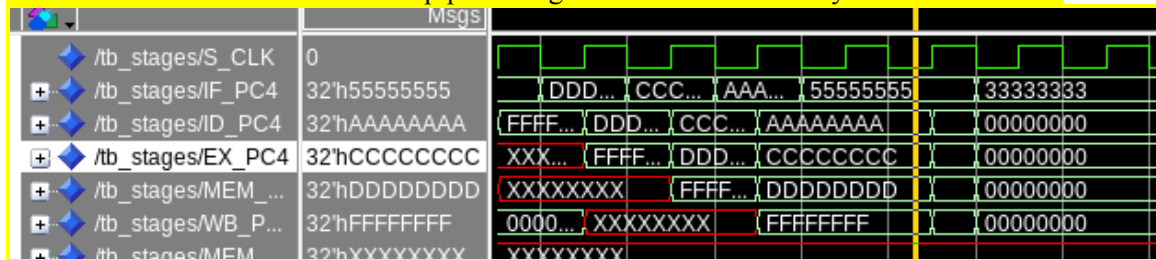[2.a.iii] Create a testbench that instantiates all four of the registers in a single design. Show that values that are stored in the initial IF/ID register are available as expected four cycles later, and



that new values can be inserted into the pipeline every single cycle. Most importantly, this testbench should also test that each pipeline register can be individually stalled or flushed.



The cursor is hovering over a stall instruction, which correctly stalls every stage for 1 cycle. After the stall, a reset (flush) is called, which clears out the values from all the stages.

Called `tb_MipsProcessor.vhd`.

[2.b.i] list which instructions produce values, and what signals (i.e., bus names) in the pipeline these correspond to.

Instruction Format	Instruction Type	Instruction	Produced Values	Pipeline Signals
R-Type	Arithmetic and Logical	add, addu	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
I-Type	Arithmetic and Logical	addi, addiu	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
R-Type	Arithmetic and Logical	sub, subu	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
R-Type	Arithmetic and Logical	and, or, xor, nor	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
I-Type	Arithmetic and Logical	andi, ori, xori	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
R-Type	Arithmetic and Logical	sll	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
I-Type	Arithmetic and Logical	slli	s_ALUOut, s_ALUB	s_ALUOp, s_RegWr
R-Type	shift	sll, srl, sra	s_ALUOut, s_ALUB	s_ALUOp, s_ShiftDirection, s_ShiftType, s_RegWr
I-Type	Mem Access	lw, lh, lhu, lb, lbu	s_ForwardA, s_ForwardB	s_memToReg, s_ALUSrc, s_WE, s_muxRegWr, s_ALUOp
I-Type	Mem Access	lui	s_RegA, s_ForwardA	s_memToReg, s_ALUSrc, s_WE, s_muxRegWr, s_ALUOp
I-Type	Mem Access	sw	No "Produced Value", but it updates a memory address with new content	s_ALUSrc, s_Stall, s_MemWr
J-Type	Control Flow	j	BranchToMux	s_J, s_Jump,
J-Type	Control Flow	jr	BranchToMux	s_Jr, s_Jump,
J-Type	Control Flow	jal	BranchToMux	s_Jal, s_Jump,
J-Type	Control Flow	beq, beq	BranchToMux	s_Branch, s_Jump, s_Signed, s_Beq

[2.b.ii] List which of these same instructions consume values, and what signals in the pipeline these correspond to.

Instruction Type	Instruction	Consumed Values	Pipeline Signals
Arithmetic and Logical	add, addu	Values from rs and rt	s_rs, s_rt
Arithmetic and Logical	addi, addiu	Value from rs and immediate	s_rs, imm
Arithmetic and Logical	sub, subu	Values from rs and rt	s_rs, s_rt
Arithmetic and Logical	and, andi	Values from rs and rt/imm	s_rs, s_rt/imm
Arithmetic and Logical	or, ori	Values from rs and rt/imm	s_rs, s_rt/imm
Arithmetic and Logical	xor, xori	Values from rs and rt/imm	s_rs, s_rt/imm
Arithmetic and Logical	nor	Values from rs and rt	s_rs, s_rt
Arithmetic and Logical	sll, slli	Values from rs and rt/imm	s_rs, s_rt/imm
Shift	sll, srl, sra	Value from rt and shift amount	s_rt, shamt
Shift	sllv, srlv, sra	Values from rs and rt	s_rs, s_rt
Memory Access	lw, lh, lhu, lb, lbu	Base address (rs) and offset	s_rs, imm
Memory Access	sw	Base address (rs) and data (rt)	s_rs, s_rt
Control Flow	jr	Jump address from rs	s_rs
Control Flow	beq, bne	Values from rs and rt	s_rs, s_rt

[2.b.iii] generalized list of potential data dependencies. From this generalized list, select those dependencies that can be forwarded (write down the corresponding pipeline stages that will be forwarding and receiving the data), and those dependencies that will require hazard stalls.

#### Load-Store:

Data dependencies can come up when a store instruction comes right after a load instruction. The store instructions need data to be loaded in the previous cycle.

#### Immediate to Immediate:

Dependencies can happen when the oneImmediate uses the result from the other.

#### Register to Register to Register:

Dependencies exist when multiple register-using instructions need the register results or use the same registers in different instructions.

#### Register to Register:

Dependencies can exist between two register-using instructions.

#### Immediate to Register:

Dependencies can come up when an immediate instruction writes to a register that a following register-using instructions will need the result.

[2.b.iv] global list of the datapath values and control signals that are required during each pipeline stage

IF/ID STAGE		ID/EX STAGE		EX/MEM STAGE		MEM/WB STAGE	
Inputted Signal	New Signals	Inputted Signal	New Signals	Inputted Signal	New Signals	Inputted Signal	New Signals
MemToReg	ReadData1	MemToReg	ALUZero	MemToReg	BranchToMux	MemToReg	MemToRegMux
Branch	ReadData2	Branch	ALUResult	Branch	DataOut	RegWrite	MEMWBRegRD
AluSrc	immExt	AluSrc	AddressToMux	MemWrite	EXMEMRegRD	DataOut	
AluOp		AluOp	FwdBOut	MemRead		ALUResult	
MemWrite		MemWrite	RegisterRD	RegWrite		RegisterRD	
RegWrite		RegWrite		PCSrc			
PCSrc		PCSrc		ALUZero			
RegDst		RegDst		ALUResult			
PC+4		ReadData1		ReadData2			
Imm		ReadData2		FwdBOut			
Address		PC+4		PC+4			
Opcode		immExt		RegisterRD			
rs		rs					
rt		rt					
rd		rd					
shamt		shamt					
funct		funct					

[2.c.i] list all instructions that may result in a non-sequential PC update and in which pipeline stage that update occurs.

Instruction	Instruction Type	Pipeline Stage	Reason for Non-Sequential PC Update
j	Jump	Decode (ID)	PC updated to the jump target address (computed from instruction).
jal	Jump and Link	Decode (ID)	PC updated to the jump target address; return address stored in \$ra.
jr	Jump Register	Execute (EX)	PC updated to the address stored in rs.
jalr	Jump and Link Register	Execute (EX)	PC updated to the address in rs; return address stored in \$ra.
beq	Branch on Equal	Execute (EX)	PC updated to branch target if $rs == rt$ .
bne	Branch on Not Equal	Execute (EX)	PC updated to branch target if $rs \neq rt$ .
bltz	Branch on Less Than 0	Execute (EX)	PC updated to branch target if $rs < 0$ .
bgez	Branch on Greater/Equal	Execute (EX)	PC updated to branch target if $rs \geq 0$ .
beql	Branch on Equal Likely	Execute (EX)	Similar to beq, but skips next instruction if branch condition is false.
bnel	Branch on Not Equal Likely	Execute (EX)	Similar to bne, but skips next instruction if branch condition is false.

[2.c.ii] For these instructions, list which stages need to be stalled and which stages need to be squashed/flushed relative to the stage each of these instructions is in.

Stages Stalled: ID/EX

Stages Squashed/Flushed: IF/ID, ID/EX, EX/MEM

For the instructions BNE, BEQ, J, JAL, and JR that result in a non-sequential PC update, the following stages need to be stalled and squashed/flushed relative to the stage each instruction is in:

Stalling:


- Stalling occurs for 1 cycle.
- The IF/ID pipeline register is stalled to prevent the next instruction from entering the Decode (ID) stage.
- The ID/EX pipeline register is stalled to prevent the instruction in the Decode (ID) stage from moving to the Execute (EX) stage.

Flushing:

- Flushing occurs for 1 cycle.
- Flushing takes place in the Fetch (IF) stage to discard the instruction that was fetched based on the sequential PC.
- Instructions producing values on the ALU Result signal in the execute stage:
  - add, addi, addiu, addu
  - sub, subu
  - and, andi
  - or, ori
  - xor, xori
  - nor
  - slt, slti
  - sll, srl, sra
- Instructions producing/using values on the mem data signal in the memory stage:
  - lw, lh, lhu, lb, lbu (load instructions)
  - sw, sh, sb (store instructions)
- Instructions producing values on the branchLogic signal going into the fetch logic unit:
  - beq, bne
- Instructions producing values on the JumpLogic and JregLogic signals going into the fetch logic unit:
  - j, jal
  - jr (uses iJreg signal specifically for register jumping)

[2.d] implement the hardware-scheduled pipeline using only structural VHDL. As with the previous processors that you have implemented, start with a high-level schematic drawing of the interconnection between components.

Hardware Diagram

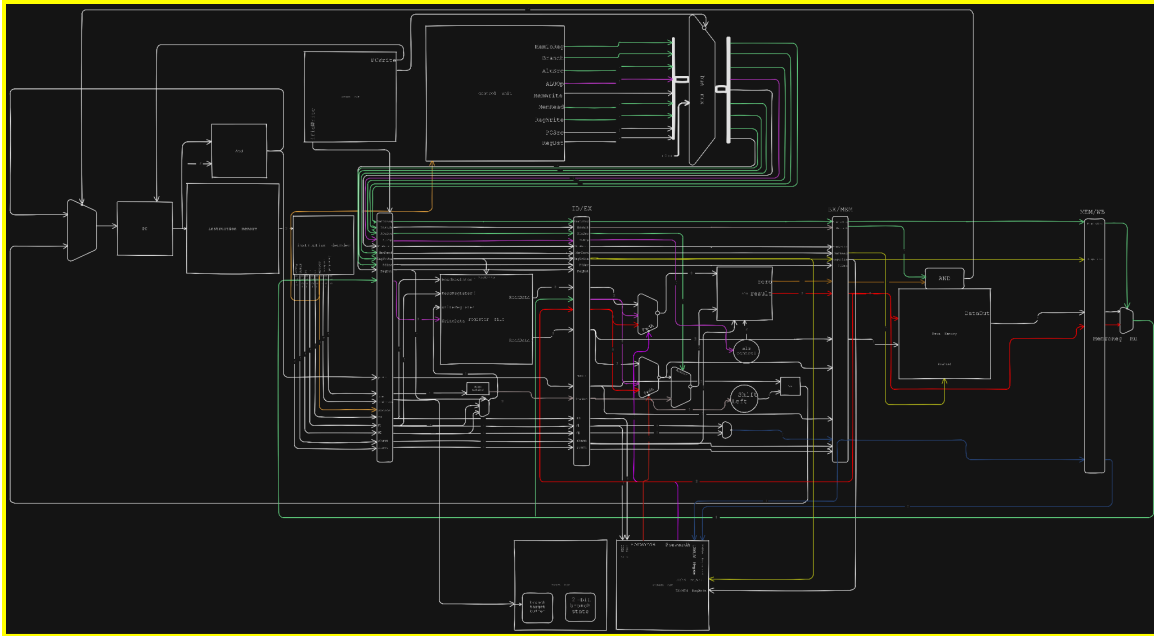

Implemented in source\_hw

[2.e – i, ii, and iii]

In your writeup, show the Modelsim output for each of the following tests, and provide a discussion of result correctness. It may be helpful to also annotate the waveforms directly




add \$11, \$1, \$2 # \$11 = \$1 + \$2 (1+2 = 3)

addu \$12, \$3, \$4 # \$12 = \$3 + \$4 (3+4 = 7)


sub \$13, \$11, \$5 # \$12 = \$11 - \$5 (3-5 = -2) RegToReg Hazard Here (The cursor is over this instruction)

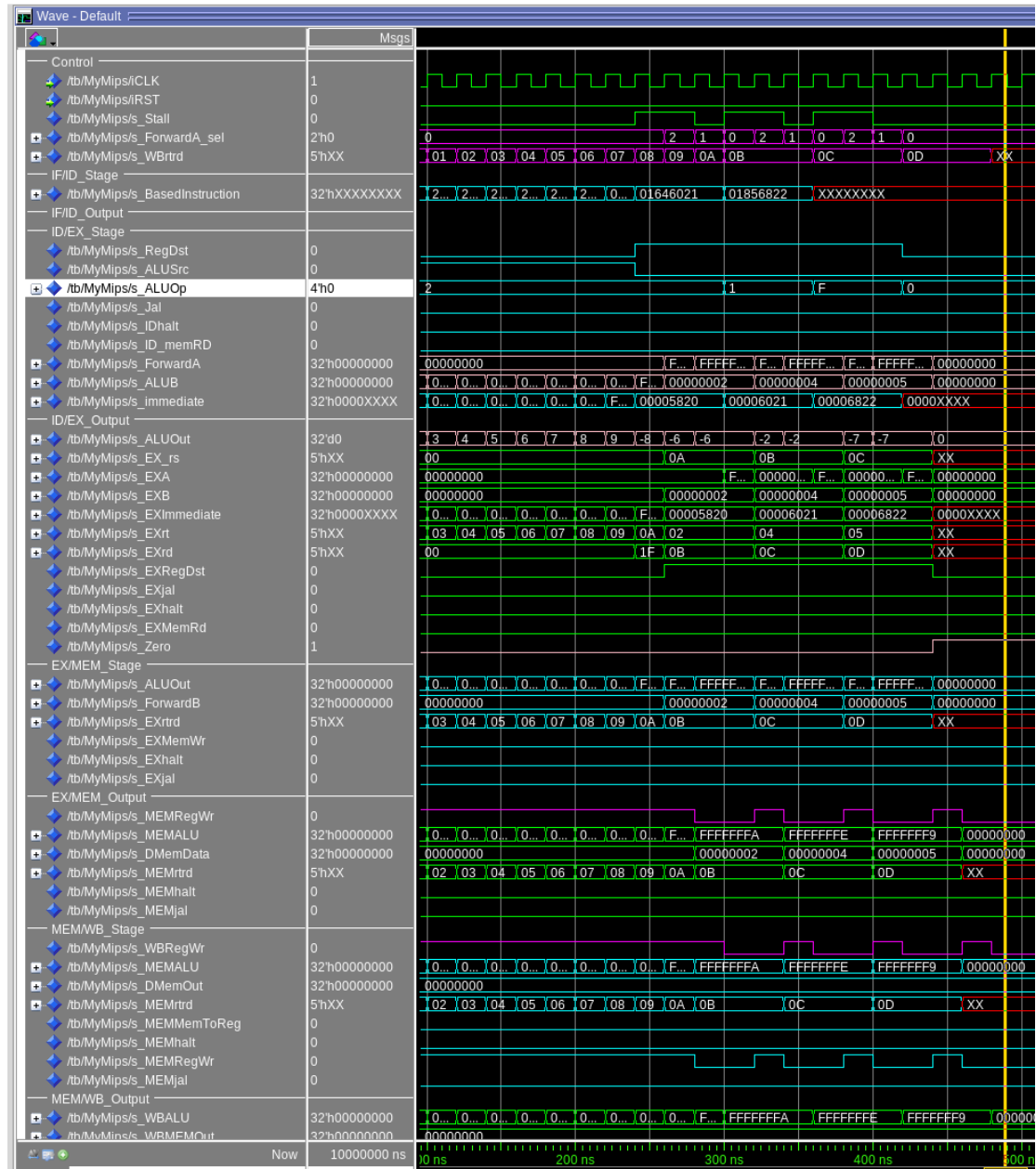The processor correctly detects the RegToReg Hazard, and the forwarding unit forwards the value of register 11 to the last instruction after a short stall. The forwarding unit is in magenta, and the hazard unit is in yellow near the top. Their values are pipelined properly to pass the relevant information (in this case, that register 11 ended up being equal to 3) to the appropriate location




This image is of RegToRegToReg.s, which is testing the RegToRegToReg Hazard, In this case, there are multiple stalls that are correctly handled. You can see the forwarding unit in purple. Each line below has a hazard except for the addi. The processor needs to stall for two cycles each, which is correctly handled. These are all ReadAfterWrite Hazards.
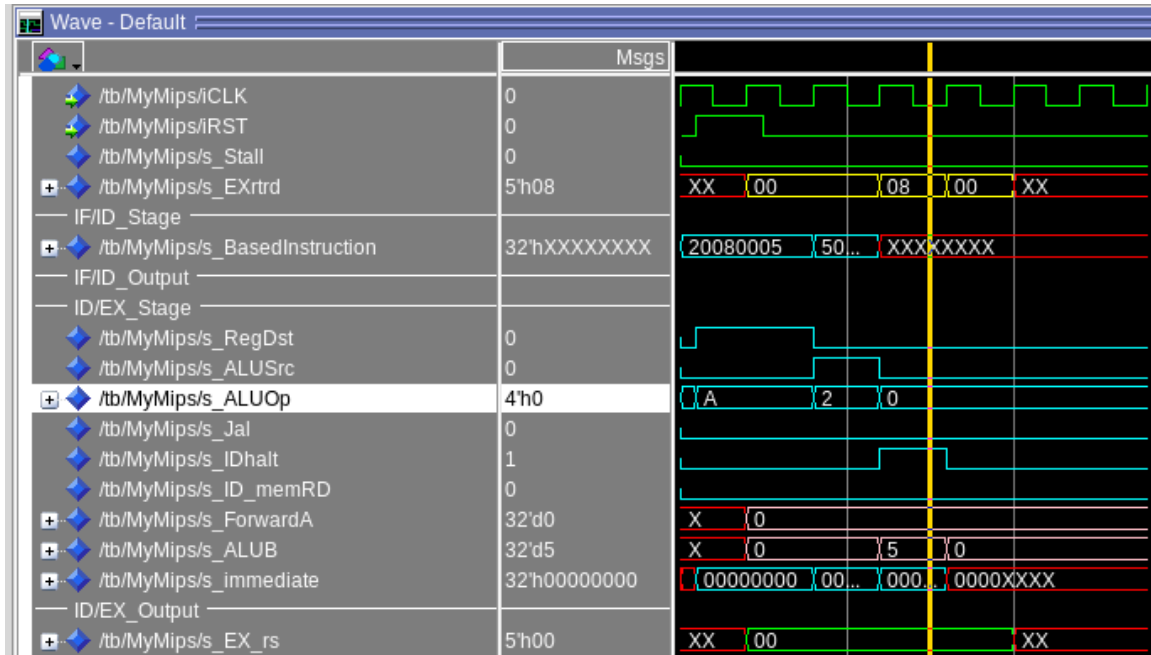
```
addi $10, $0, -8      # Place "10" in $10
add  $11, $10, $2      # $11 = -8 + 2 = -6 RAW
addu $12, $11, $4      # $12 = -6 + 4 = -2 RAW
sub  $13, $12, $5      # $12 = -2 - 5 = -7 RAW
```



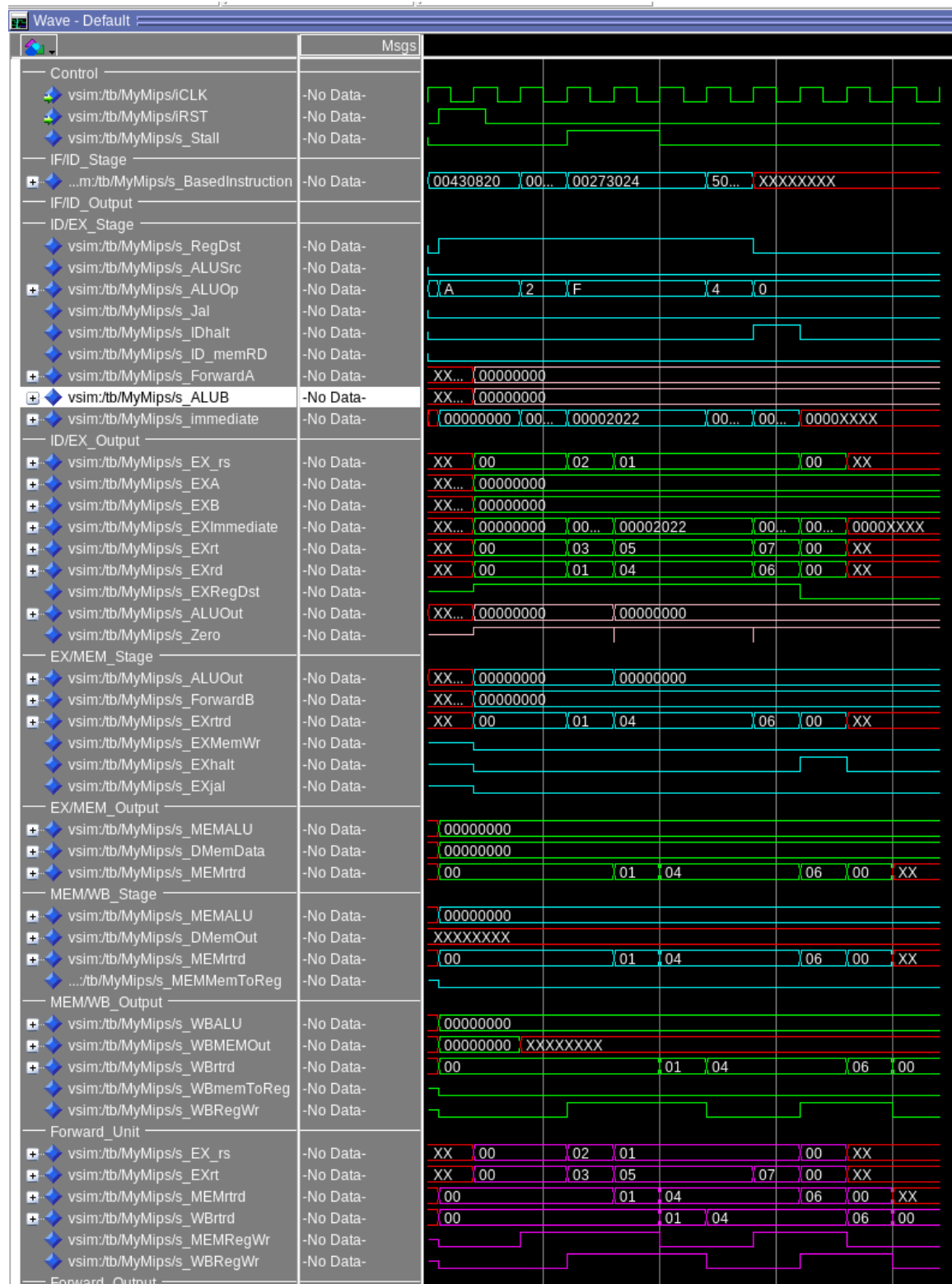In this image, I have ImmtoImm.s shown. this just runs one instruction: addi \$t0, \$zero, 5. This is problematic, as If it were possible to change the set value of 0 to something else, it could cause major issues. Our processor handles this instruction as a nop, as it doesn't actually change any values in memory or in the register file. Hazard Detector unit signal is shown in yellow.




Here is a WAR Hazard Getting Detected. I used WAR.s in my MIPS programs, which ran the instructions below. It properly detects the hazard and forwards anything relevant, as well as running a stall.


add \$1, \$2, \$3

sub \$3, \$4, \$5

and \$6, \$3, \$7

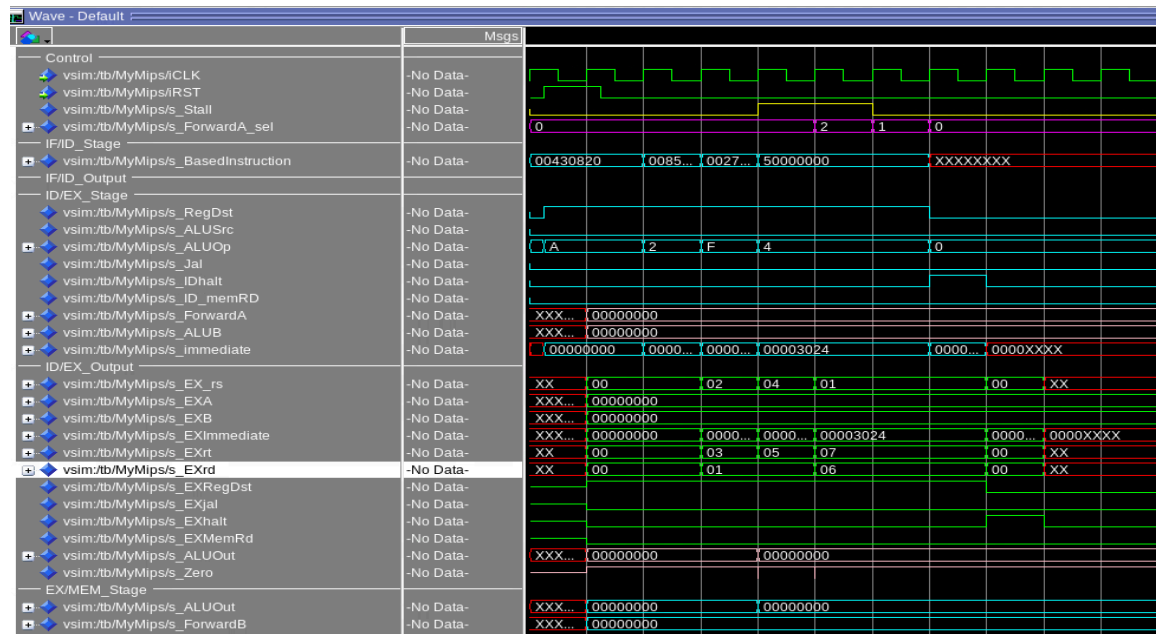


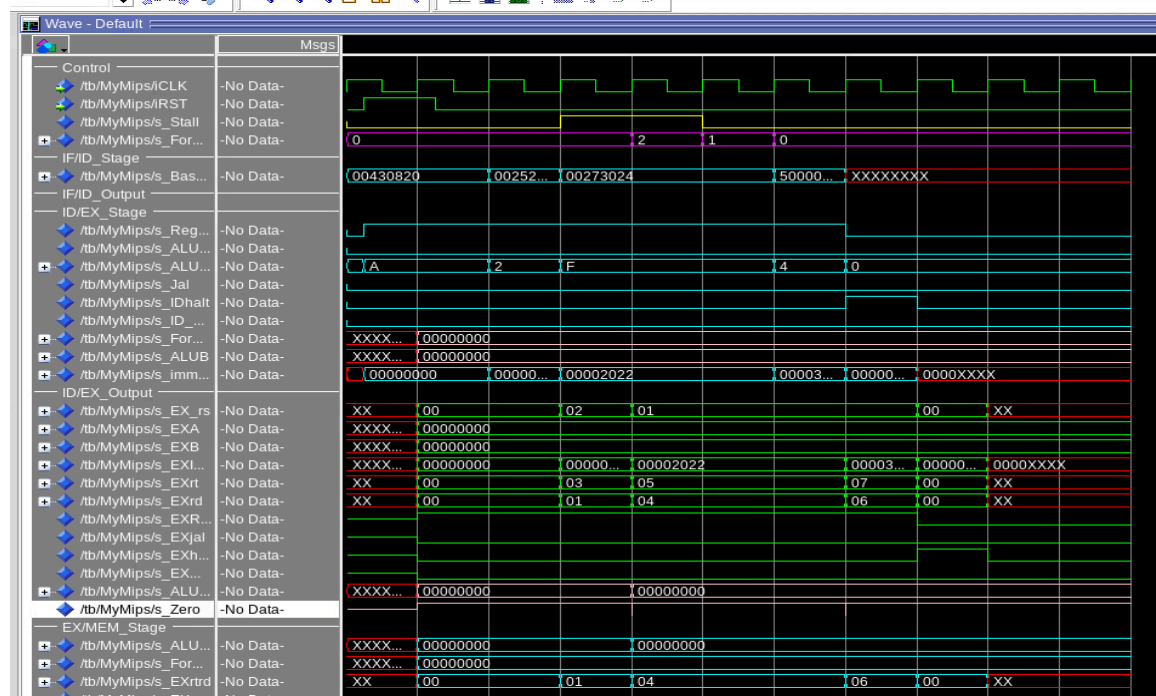Here is a WAW hazard being detected. A stall is used to allow time for the forwarding unit to forward the value that is depended on. Stall is shown in yellow, and the forwarded register is shown in magenta



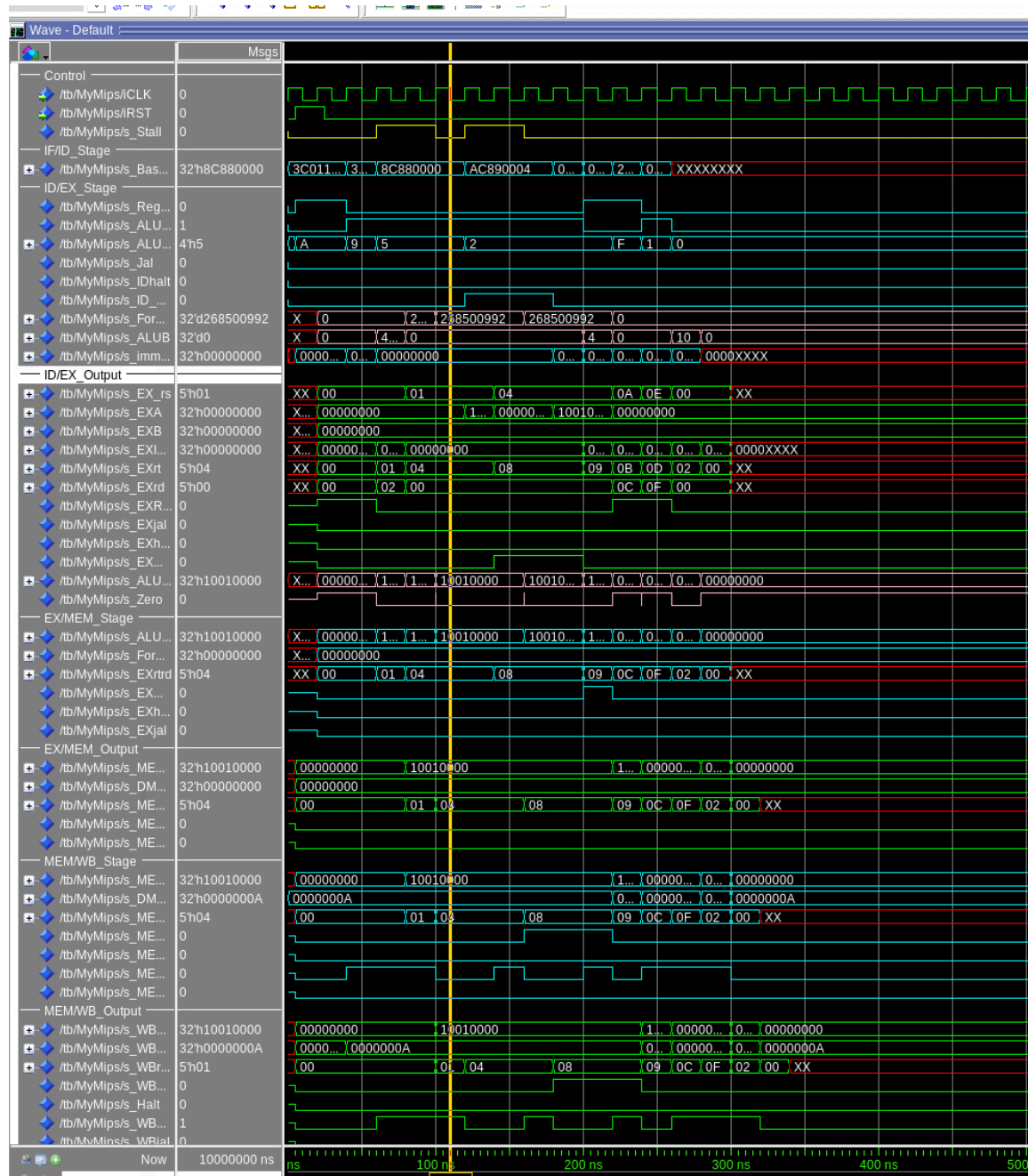
Here is a RAW hazard being detected (RAW.s) A stall is used to allow time for the forwarding unit to forward the value that is depended on. Stall is shown in yellow, and the forwarded register is shown in magenta





Here is an implementation of a Structural Hazard, as the LW and SW instructions rely on the register file at the same time, so we have to stall. The stall is in yellow at the top.
 
```
la $a0, array      # Load the address of the $a0 array
lw $t0, 0($a0)     # Load the first word from the array into $t0
sw $t1, 4($a0)     # Store the value from $t1 into the second word of the array
add $t4, $t2, $t3   # Add $t2 and $t3, storing the result in $t4
sub $t7, $t6, $t5   # Subtract $t5 from $t6, storing the result in $t7
```



Here is an implementation of a control hazard. In this case, no stalls were needed, but an instruction did need to get flushed from the pipeline. This is because the next instruction got loaded, and then the Hazard Detection realized that the instruction shouldn't have ever been loaded, so it wipes it from the pipeline.

```

beq $1, $2, Label
add $3, $4, $5
sub $6, $7, $8
beq $1, $2, Label
Label:
or $9, $1, $2
halt


```

[2.e.i]

Create a spreadsheet to track these cases and justify the coverage of your testing approach. Include this spreadsheet in your report as a table.

A	B	C	D
Hazard	MIPS File	Instructions Example	Justification
WAR Hazard	WAR.s	add \$1, \$2, \$3 sub \$3, \$4, \$5 and \$6, \$3, \$7	For all three of these, we need to insure that forwarding paths are implemented properly to minimize the length of pipeline stalls
RAW Hazard	RAW.s	add \$1, \$2, \$3 sub \$4, \$1, \$5 and \$6, \$1, \$7	
WAW Hazard	WAW.s	add \$1, \$2, \$3 sub \$1, \$4, \$5 and \$6, \$1, \$7	
Structural Hazard	StructHaz.s	lw \$1, 0(\$2) sw \$1, 4(\$3) add \$4, \$1, \$5	Tests resource conflicts, priorities must be assigned or maintained. Stalls must be kept at a minimum
Control Hazard	CtrlHaz.s	beq \$1, \$2, Label add \$3, \$4, \$5 sub \$6, \$7, \$8 Label: or \$9, \$1, \$2 jr \$ra	Corrects issues with incorrect speculation or assumptions. Validate branch decisions

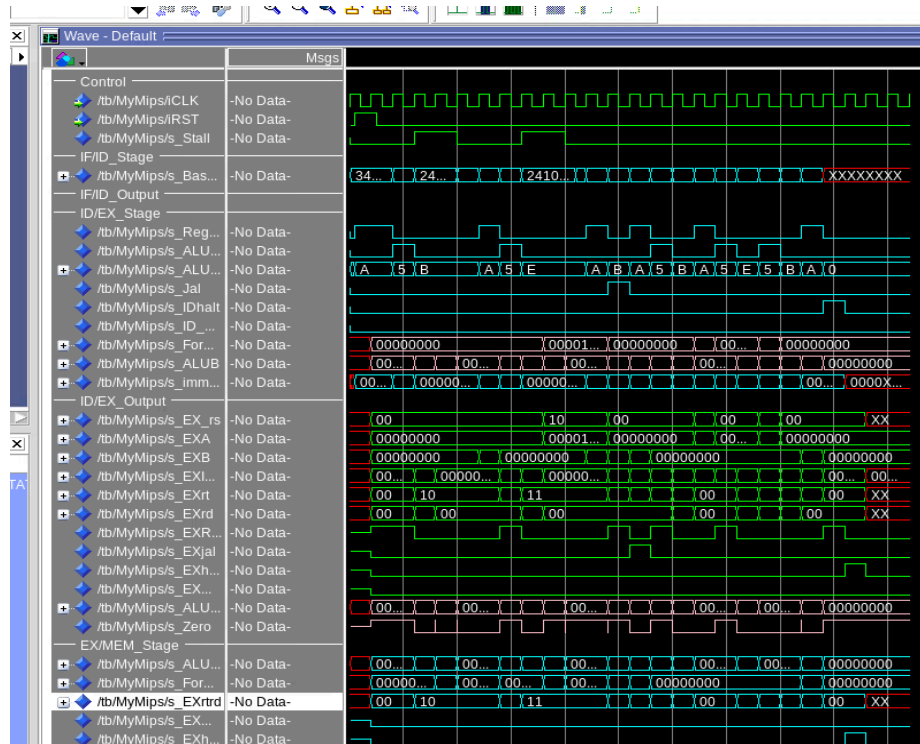Create a spreadsheet to track these cases and justify the coverage of your testing approach. Include this spreadsheet in your report as a table.



[2.e.iii]

Here is our simplebranch.s implementation from Project1, which is the script shown to the right. The signals below show that the new system is able to run all those instructions pipelined, although the hazard detection system has to work really hard. there are numerous flushes, stalls, and forwarded values that are done to make some of the instructions work more efficiently

```
main:
    ori $s0, $zero 0x1234
    j skip
    li $s0 0xffffffff


skip:
    ori $s1 $zero 0x1234
    beq $s0 $s1 skip2
    li $s0 0xffffffff

skip2:
    jal fun
    ori $s3 $zero 0x1234

    beq $s0, $zero exit
    ori $s4 $zero 0x1234
    j exit

fun:
    ori $s2 $zero 0x1234
    jr $ra


exit:
    halt
```

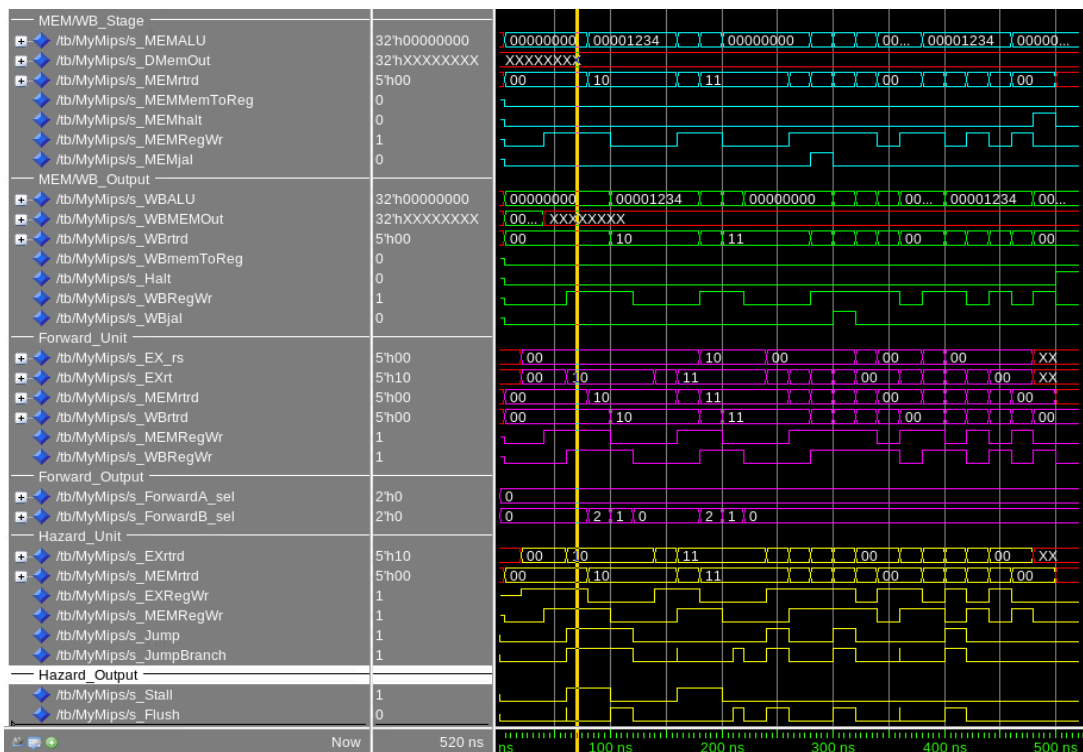

```

** Observed: b'DQ/\xbduh-\xf9\xec\xb3\xdc\x10\xc2\x
All VHDL src files compiled successfully
Testing file: ../src_sc/proj/mips/fibonacci.s
Mars simulation: pass
Modelsim simulation: pass
Test Result: pass
Mars Instructions: 330
Processor Cycles: 560
CPI: 1.7
Results in: output/fibonacci.s

```

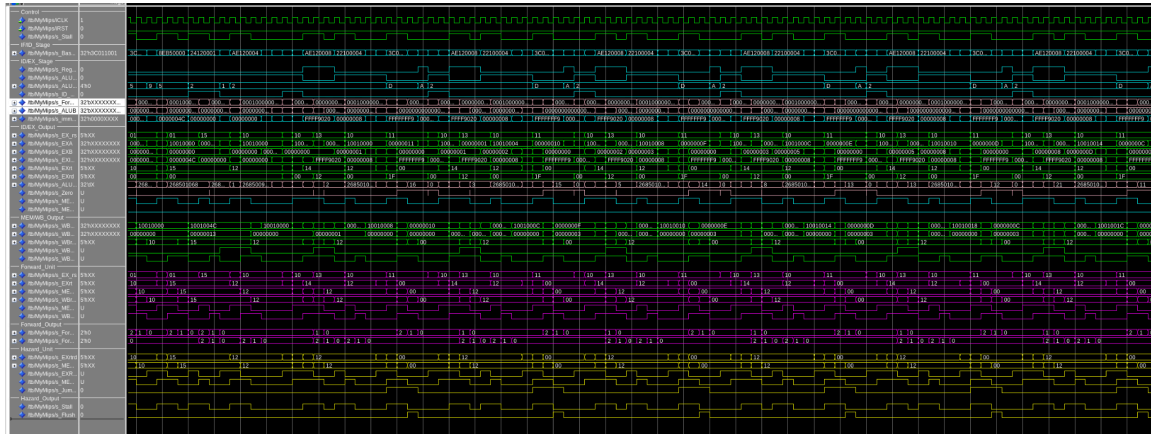

Here is the implementation of the Fibonacci Sequence. It carried over without any changes, and works significantly faster than it did previously. The hazard detection unit has to work extremely hard, as there are a lot of jumps and branches involved in the code itself which results in a lot of stalls and flushes.

The Forwarding unit is Magenta, the Hazard Detection Unit is Yellow, and the ALU is pink.

```

# Compute several Fibonacci numbers and put in array, then print
.data
fibn: .word $0, 1, 1B # "array" of words to contain fib values
size: .word 10 # size of "array" (agrees with array declaration)
.prompt: .asciiz "How many Fibonacci numbers to generate? (2 <= n <= 10)"
.text
li $0b, fibn # load address of array
la $a5, size # load address of size variable
lw $a5, 0($a5) # load array size

# Optional: user inputs the number of Fibonacci numbers to generate
# $v0: la $v0, .prompt # load address of prompt for syscall
# li $v0, 4 # specify Print String service
# syscall # print the prompt string
# li $v0, 0 # specify Read Integer service
# syscall # read the number, after this instruction, the number read is in $v0
# bgt $v0, $a5, pr # Check boundary on user input -- if invalid, restart
# btl $v0, $zero, pr # Check boundary on user input -- if invalid, restart
# add $a5, $v0, $zero # transfer the number to the desired register

li $a2, 1 # $1 is the known value of first and second Fib. number
sw $a2, 0($a5) # F[0] = 1
sw $a2, 4($a5) # F[1] = F[0] + 1
addi $a1, $a5, -2 # Counter for loop, will execute (size-2) times

# Loop to compute each Fibonacci number using the previous two Fib. numbers.
loop: lw $a3, 0($a5) # Get value from array F[n-2]
lw $a4, 4($a5) # Get value from array F[n-1]
add $a2, $a3, $a4 # F[n] = F[n-1] + F[n-2]
sw $a2, 4($a5) # Store newly computed F[n] in array
addi $a5, $a5, 4 # Increment address to now-known Fib. number storage
addi $a1, $a1, -1 # decrement loop counter
bne $a1, $zero, loop # Repeat while not finished

# Fibonacci numbers are computed and stored in array. Print them.
la $a0, fibn # first argument for print (array)
add $a1, $zero, $a5 # second argument for print (size)
jal print # call print routine.

# The program is finished. Exit.
halt
j die

#####
# Subroutine to print the numbers on one line.
.data
space: .asciiz " " # space to insert between numbers
head: .asciiz "The Fibonacci numbers are:\n"
.text
print: add $t0, $zero, $a0 # starting address of array of data to be printed
add $t1, $zero, $a1 # initialize loop counter to array size
la $a0, head # load address of the print heading string
ori $a0, $a0, 4 # specify Print String service
syscall # print the heading string

out: lw $a0, 0($t0) # load the integer to be printed (the current Fib. number)
ori $a0, $a0, $zero, 1 # specify Print Integer service
syscall # print Fibonacci number

la $a0, space # load address of space for syscall
ori $a0, $a0, $zero, 4 # specify Print String service
syscall # print the space string

addi $t0, $t0, 4 # increment address of data to be printed
addi $t1, $t1, -1 # decrement loop counter
bne $t1, $zero, out # repeat while not finished

jr $ra # return from subroutine

die:
# End of subroutine to print the numbers on one line.
#####

```

[2.f]

report the maximum frequency your hardware-scheduled pipelined processor can run at and determine what your critical path is (specify each module/entity/component that this path goes through).

```
FMax: 48.38mhz
```

```
From Node      :
```

```
mem:DMem|altsyncram:ram_rtl_0|altsyncram_eg81:auto_generated|ram_block1a0~porta_we_reg
```

```
To Node        :
```

```
EX_MEM:instEXMEM|dffg:\G_ALU_Reg:31:ALUDFFGI|s_Q
```

48.38 was our maximum frequency for our hardware implementation. As for our critical path, we inferred from the synthesis output that;